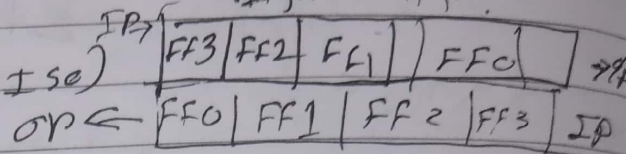


# # Register

To increase the storage capacity in terms of no. of bits we have to use a group of flip-flops. Such a group of flip-flops are known as registers.   
 Left Shift Right Shift

1) Serial In Serial out (SISO)





2) SIPO

3) PISO

4) PIPO




Left Shifts

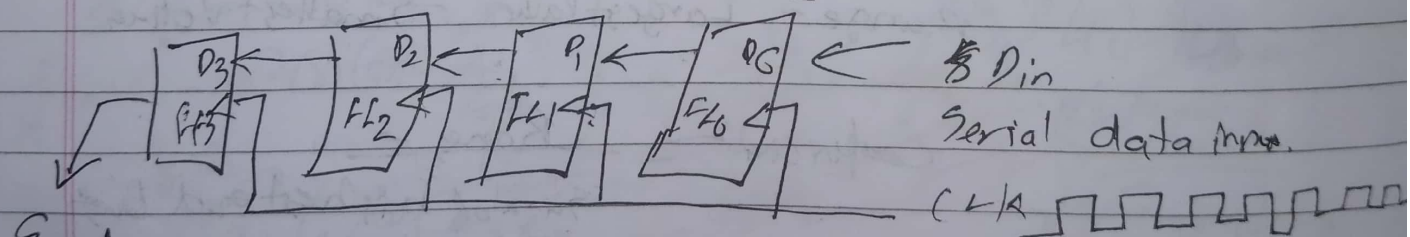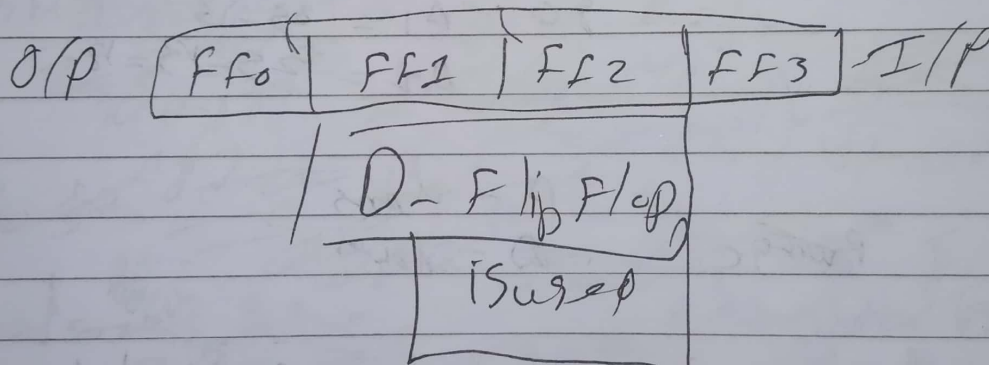

Serial data Output

Q3	Q2	Q1	Q0
0	0	0	0
0	0	0	1
0	0	1	0
0	1	0	0
1	0	0	0

CLK	Q3	Q2	Q1	Q0	D0
Initially	0	0	0	0	
	0	0	0	0	1
↓	0	0	0	0	1
↓	0	0	0	1	1
↓	0	0	1	1	1
↓	0	1	1	1	1
↓	1	1	1	1	1

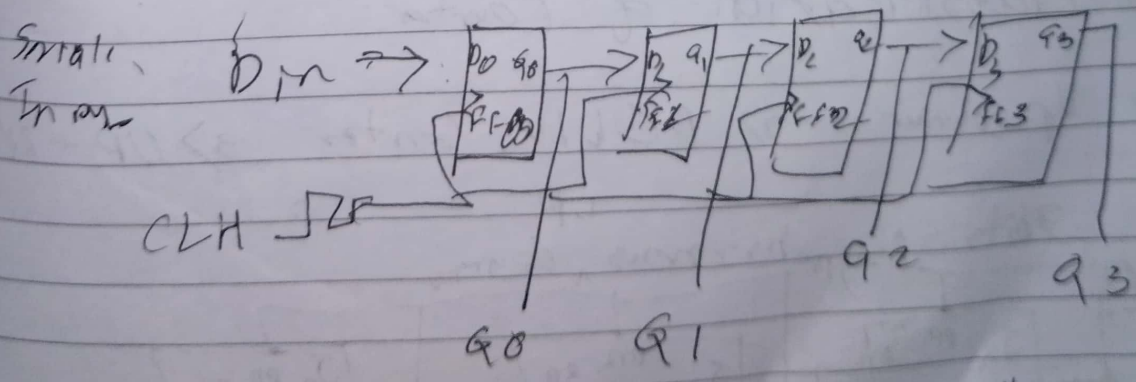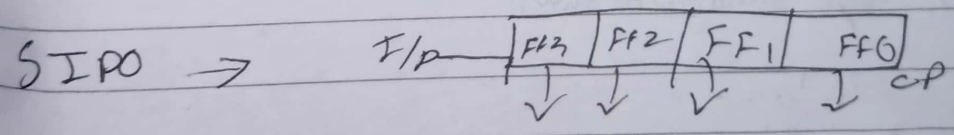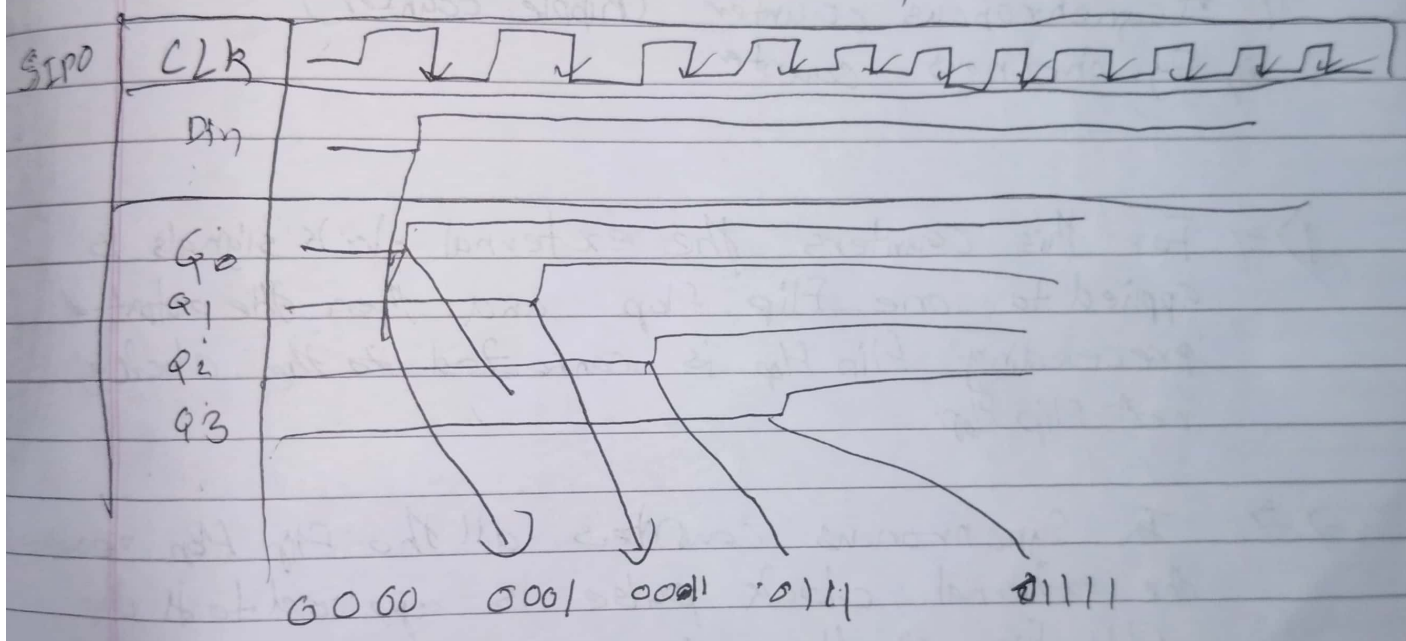

- ① In this operation the data is entered serially and taken out parallel as shown in figure.
- ② 1st the data is loaded bit by bit. Then outputs



Now Right to Left

③ As soon as the loading is complete and all the flip flops contact the required data the outputs are enabled so that all the data is made available simultaneously

### Counters.

A digital circuit. used for counting pulses is known as counters and its a sequential ~~output~~ circuit.


- 1) Asynchronous counter (Ripple counter)
- 2) Synchronous counter.

1)  $\Rightarrow$  For this counters the external clock signals is applied to one Flip flop and then the output of preceeding Flip Flop is connected to the clock of next Flip Flop.

2)  $\Rightarrow$  In Synchronous counters all the flip flop receive the external clock pulse is applied to all the Flip Flop simultaneously.

### \* Classification of counter

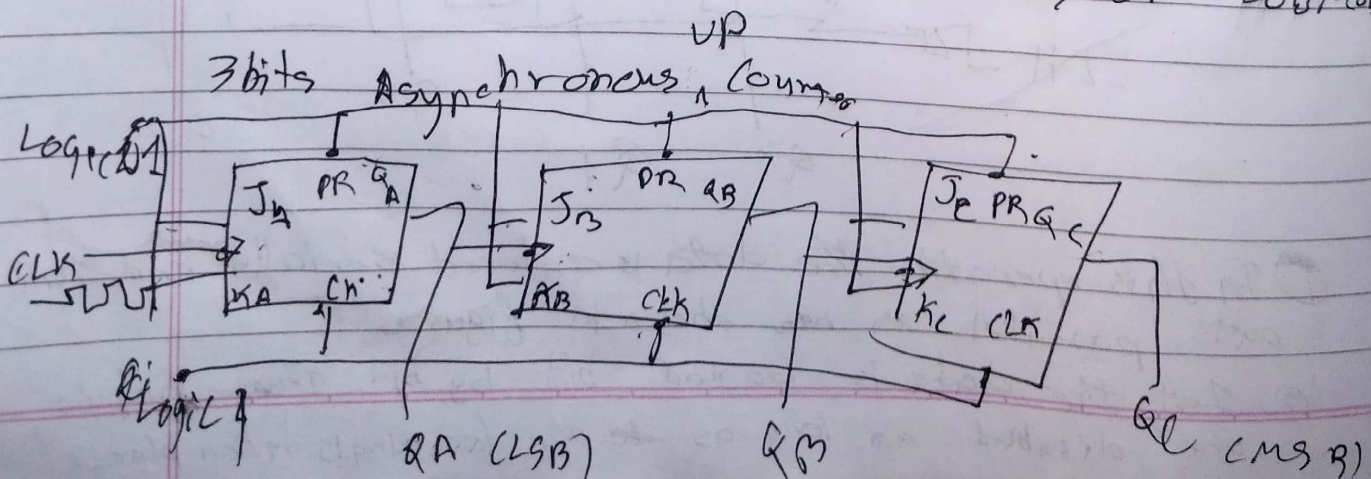- 1) Up counter
- 2) DOWN counter
- 3) UP - DOWN counter






$Q_C \ Q_B \ Q_A$   
 0 0 0  
 0 0 1  
 0 1 0  
 0 1 1

CLK	$Q_C$	$Q_B$	$Q_A$	state	D. E
	0	0	0	1	0
↓	0	0	1	2	1
↓	0	1	0	3	2
↓	0	1	1	4	3
↓	1	0	0	5	4
↓	1	0	1	6	5
↓	1	1	0	7	6
↓	1	1	1	8	7
↓				9	

3 bit asynchronous down Counter

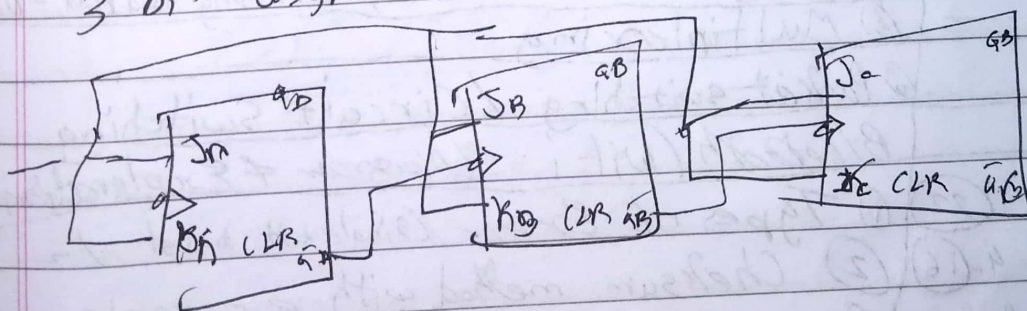

Up-down-counter